

MLV TEXTILE ENGG COLLAGE BHILWARA

Department of Electronics and Communication Engg


First midterm question paper with answer

Session (2017-18)

Subject - circuit analysis and synthesis

Q.1 Derive the current relation in R-L series circuit when a dc, ac, step, ramp, impulse signal connect at time $t=0$, assume initial condition are zero

Sol.1

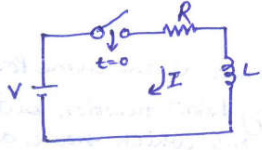

Consider a series RL circuit shown in fig. Initial value of current is zero before switch closed. by applying KVL we get

$$L \frac{dI}{dt} + RI = V$$

$$\frac{dI}{dt} + \frac{R}{L} I = \frac{V}{L}$$


by the analysis we get

$$i = \frac{V}{R} (1 - e^{-(R/L)t})$$

by putting the i/p as DC, ac, ramp, impulse signal we get the expression. for example we get the eq^m of current for DC as above. by putting the step function we get the eq^m = $i = \frac{V}{R} [1 - e^{-(R/L)t}]$

Q.2 Derive the current relation in R-C series circuit when a dc, ac, step, ramp, impulse signal connect at time $t=0$, assume initial condition are zero.

Sol.2

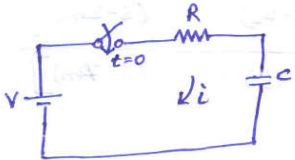

Here we have a series RC circuit shown in fig. the initial value of current is zero before switching. by applying the KVL we get

$$Ri + \frac{1}{C} \int i dt = V$$

$$R \frac{di}{dt} + \frac{i}{C} = 0$$

And by the analysis we get -

$$i(t) = -\frac{V}{R} e^{-t/RC}$$

for the DC input at the ckt similarly we can get the current relation for the ac, ramp and impulse signal.

Q.3 What do you mean by pole and zero for a network function.

Sol.2 A NW function can be written as the ratio of two Polynomials.

$$H(s) = \frac{A(s)}{B(s)} = \frac{a_0 s^m + a_1 s^{m-1} + \dots + a_m s + a_m}{b_0 s^n + b_1 s^{n-1} + \dots + b_{n-1} s + b_n}$$

$$= \frac{\frac{a_0}{b_0} [(s-z_1)(s-z_2) \dots (s-z_m)]}{[(s-p_1)(s-p_2) \dots (s-p_n)]}$$

Then z_1, z_2, \dots, z_m are the zero's and p_1, p_2, \dots, p_n are the Poles.

Q.4 Write the interrelationship of parameters

Sol. 4 Interrelationship betⁿ Parameters

Parameter	Z		Y	
Z	Z_{11}	Z_{12}	$\frac{Y_{22}}{\Delta Y}$	$-\frac{Y_{12}}{\Delta Y}$
	Z_{21}	Z_{22}	$-\frac{Y_{21}}{\Delta Y}$	$\frac{Y_{11}}{\Delta Y}$
Y	$\frac{Z_{22}}{\Delta Z}$	$-\frac{Z_{12}}{\Delta Z}$	Y_{11}	Y_{22}
	$-\frac{Z_{21}}{\Delta Z}$	$-\frac{Z_{11}}{\Delta Z}$	Y_{21}	Y_{22}


Similarly we can find the other Relation.

MLV TEXTILE ENGG COLLAGE BHILWARA

Department of Electronics and Communication Engg
 Second midterm question paper with answer
 Session (2017-18)
 Subject - circuit analysis and synthesis

Q 1. Derive the current relation in R-L series circuit when a dc, ac, step, ramp, impulse signal disconnect at time $t=0$, assume initial condition.

Sol 3

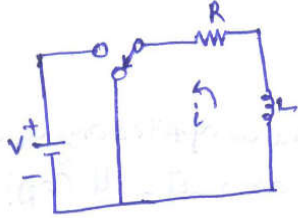


Now we circuit the i/p is disconnected at time $t=0$, and we assume that initial condition is not zero then eqⁿ for ckt will be $Ri + L \frac{di}{dt} = 0$ at $t=0$.

than by the analysis we get $i = \frac{V}{R} e^{-t/\tau} = 0.368 I_0$

Q.2 Derive the current relation in R-C series circuit when a dc, ac, step, ramp, impulse signal disconnect at time $t=0$, assume initial condition

Sol 4

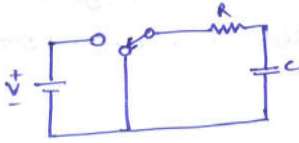

Here we have the ckt, the i/p is disconnected at time $t=0$, and we assume that initial condition is not zero than the eqⁿ

$$Ri + \frac{1}{C} \int i \cdot dt = 0$$

and by the analysis we can get $i(t) = -\frac{V}{R} e^{-(t/RC)}$

Similarly we can derive for the other given i/p's.

Q.3 Obtain the input output impedance of a two port network in Z, Y, h & T parameters.

Sol 1 input impedance of two Port N/w are


$$Z_{in} = \frac{Z_{11}Z_{22} - Z_{12}Z_{21} + Z_{11}Z_R}{Z_{22}Z_R} \quad \text{Z Parameter}$$

$$Z_{in} = \frac{AZ_L + B}{CZ_L + D} \quad \text{ABCD or T Parameter}$$

$$Z_{in} = h_{11} - \frac{h_{12}h_{21}Z_R}{1 + h_{22}Z_R} \quad \text{h-Parameter}$$

Q.4 Explain the cascade connection of two two-port network

Solⁿ

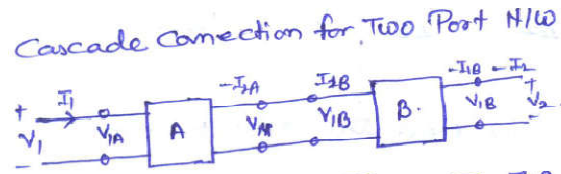

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_A & B_A \\ C_A & D_A \end{bmatrix} \begin{bmatrix} A_B & B_B \\ C_B & D_B \end{bmatrix}$$

$$[T] = [T_A] [T_B]$$